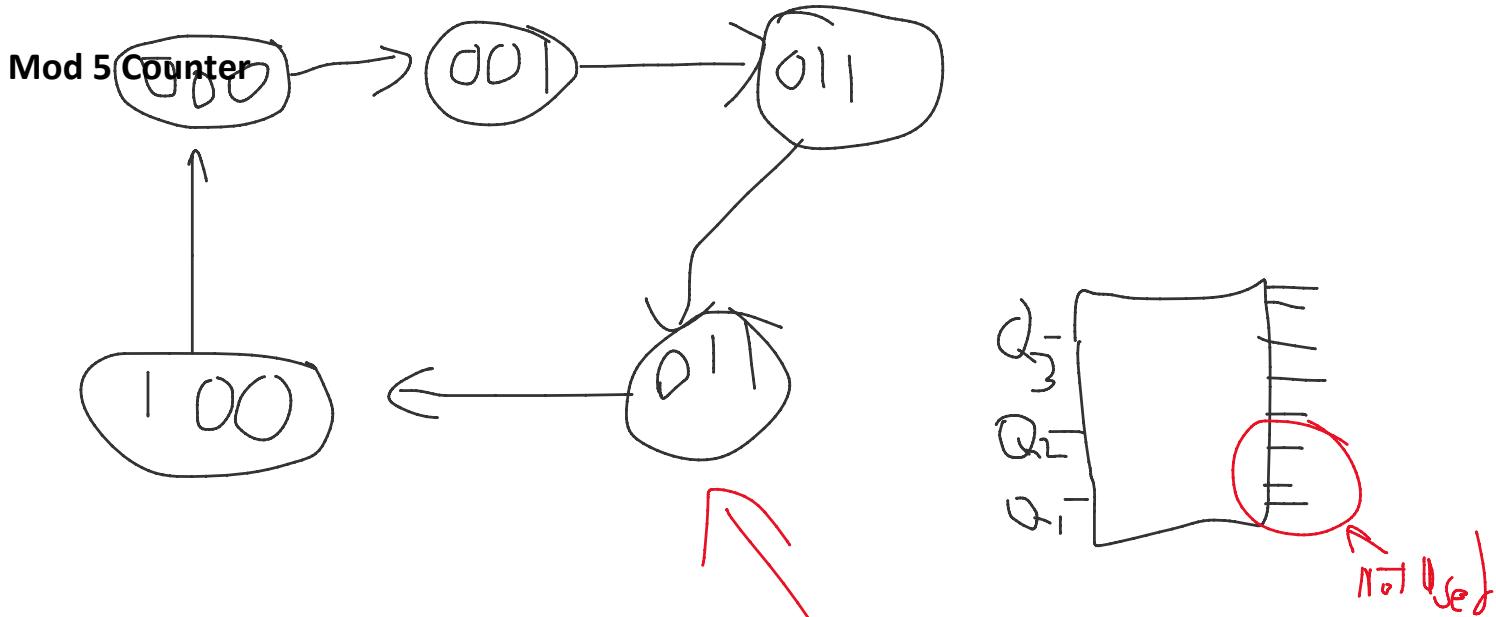


Day 5 (Jan 31st)

Sunday, February 2, 2020 2:11 AM



Q_3	Q_2	Q_1		Q_3^+	Q_2^+	Q_1^+
0	0	0		0	0	1
0	0	1		0	1	0
0	1	0		0	1	1
0	1	1		1	0	0
1	0	0		0	0	0
1	0	1		X(0)	X(1)	X(0)
1	1	0		X(0)	X(1)	X(0)
1	1	1		X(1)	X(0)	X(0)

Q_3^+ :

		Q_2	Q_2	
	0	0	1	0
Q_3	0	X	X	X
		Q_1	Q_1	

$$Q_3^+ = Q_1 Q_2$$

Make Sure to go back into the truth table and fill in the don't cares

Q_2^+ :

		Q_2	Q_2	
	0	1	0	1
Q_3	0	X	X	X
		Q_1	Q_1	

$$Q_2^+ = Q_1 Q_2 + Q_2 Q_1' \leftarrow \text{That is Exclusive Or}$$

Make Sure to go back into the truth table and fill in the don't cares


Q_1^+ :

		Q_2	Q_2	
	1	0	0	1
Q_3	0	X	X	X
		Q_1	Q_1	

$$Q_1^+ = Q_3' Q_1'$$

Make Sure to go back into the truth table and fill in the don't cares

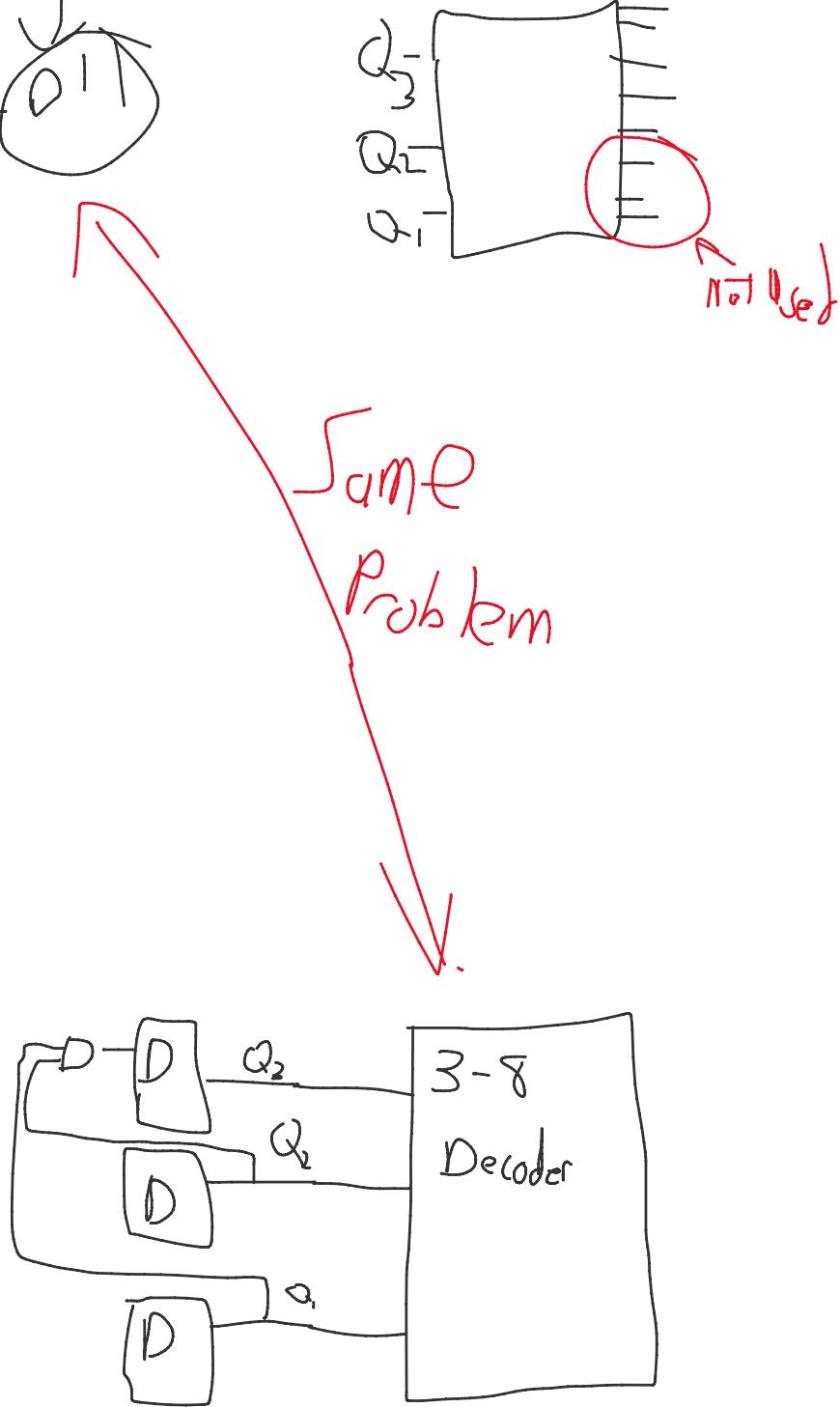These Circuits are **Self Correcting** (Even the don't care states push to a valid state without an infinite loop.



I _D	Q
0	0
1	1

Input D Flip Flop = I_D
Input T Flip Flop = I_T

I _T	Q
0	No Change
1	Complement

Q ₃	Q ₂	Q ₁		Q ₃ ⁺	Q ₂ ⁺	Q ₁ ⁺		I _{T3} ⁺	I _{T2} ⁺	I _{T1} ⁺		Q _{T3} ⁺	Q _{T2} ⁺	Q _{T1} ⁺
0	0	0		0	0	1		0	0	1		0	0	1
0	0	1		0	1	0		0	1	1		0	1	0
0	1	0		0	1	1		0	0	1		0	1	1
0	1	1		1	0	0		1	1	1		1	0	0
1	0	0		0	0	0		1	0	0		0	0	0
1	0	1		X(0)	X(1)	X(0)		X(1)	X(1)	X(0)		0	1	1
1	1	0		X(0)	X(1)	X(0)		X(1)	X(0)	X(0)		0	1	0
1	1	1		X(1)	X(0)	X(0)		X(0)	X(1)	X(0)		1	0	1

I_{T3}⁺:

			Q ₂	Q ₂	
	0	0	1	0	
Q ₃	1	X	X	X	
		Q ₁	Q ₁		

$$I_{T3}^+ = Q_3 + Q_1 Q_2$$

Make Sure to go back into the truth table and fill in the don't cares

I_{T2}⁺:

			Q ₂	Q ₂	
	0	1	1	0	
Q ₃	0	X	X	X	
		Q ₁	Q ₁		

$$I_{T2}^+ = Q_1$$


Make Sure to go back into the truth table and fill in the don't cares

I_{T1}⁺:

			Q ₂	Q ₂	
	1	1	1	1	
Q ₃	0	X	X	X	
		Q ₁	Q ₁		

$$I_{T1}^+ = Q_3'$$

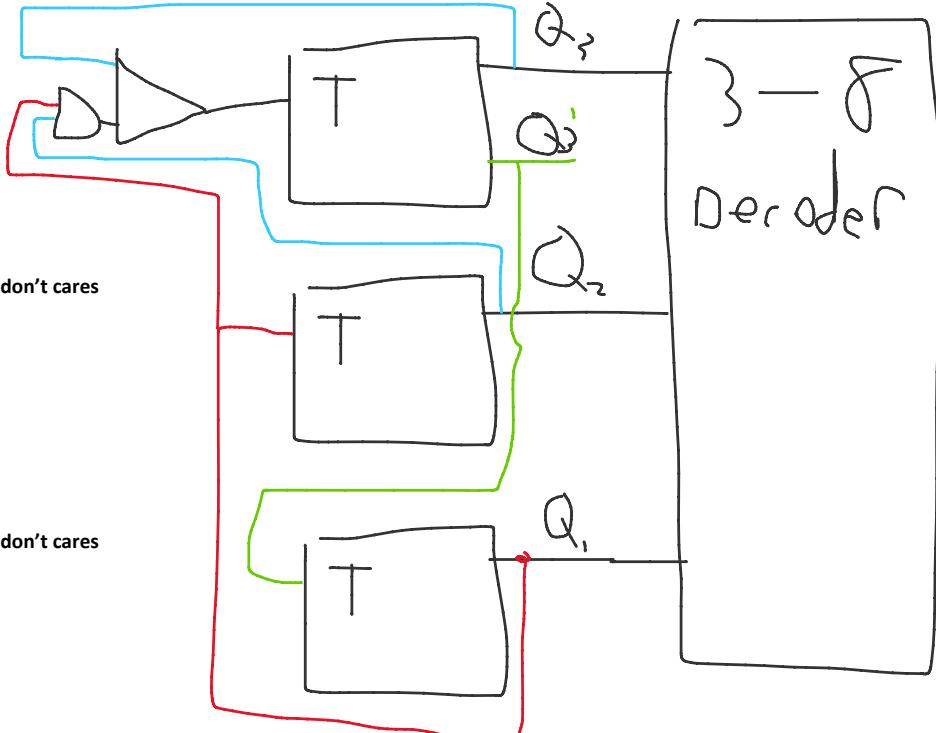Make Sure to go back into the truth table and fill in the don't cares



Multiplication:

Multiplication in the ALU takes multiple clock cycle

Signed and Unsigned are separate circuits in Multiplication

Step	C (Carry) (1 bit)	A (Answer) (4 bit)	Q (Multiplier) (4 bit)	M (First Number) (4 bit)	Operation
0	0	0000	1011	1101	Initialize
1	0	1101	1011	1101	Add M to A (0000 + 1101=)

					01101)
1.5	0	0110	1101	1101	Shift
2	1	0011	1101	1101	Add M to A (0110 + 1101= 10011)
2.5	0	1001	1110	1101	Shift
3	0	1001	1110	1101	Add Zero to A (0000 + 1001=01001)
3.5	0	0100	1111	1101	Shift
4	1	0001	1111	1101	Add M to A (1101 + 0100 = 10001)
4.5	0	1000	1111	1101	Shift

So Row 4.5 is the answer A_Q makes $10001111_b = 143$

$1101 = 13$

$1011 = 11$

$13 * 11 = 143$ So We are correct